

## EE202 Lab Report 1

Cemal Güven Adal

21703986

In this lab the goal is to find two methods to measure Q( quality factor) of an inductor. In the LTspice I have used an imaginary  $R_{in}$  to mimic the internal resistance of the inductor. Q is equal to  $WL/R_L$  , Thus quality factor changes with frequency because of the  $\omega$  component in the equation. So Q is calculated for each different frequency.

### Software Lab

#### First Method( Phase difference)

Inductors create a phase difference in the circuit. If we can measure the phase difference in the circuit we can find inductance and the resistance of the inductor. The phase difference can be measured by finding the time delays of the waveforms between  $V_{in}$  and  $V_{out}$ ,  $V_{in}$  being the waveform before the inductor and  $V_{out}$  being waveform after the inductor.

$$\Theta = 360 \times f \times \Delta t$$

The gain ratio is :

$$V_{out}/V_{in} = R_{ext}/(j\omega L + R_L + R_{ext})$$

The phase difference is

$$\phi = \tan^{-1}(\omega L / R_L + R_{ext})$$


To solve two unknowns I have used two resistors for creating two equations and then solved. First  $R_{external}$  is  $R_1$  and second is  $R_2$ .

$$\tan\phi = \omega L / (R_L + R_1)$$

$$\tan\phi_2 = \omega L / (R_L + R_2)$$


$$R_L = (\tan\phi_2 \times R_2 - \tan\phi \times R_1) / (\tan\phi_1 - \tan\phi_2)$$
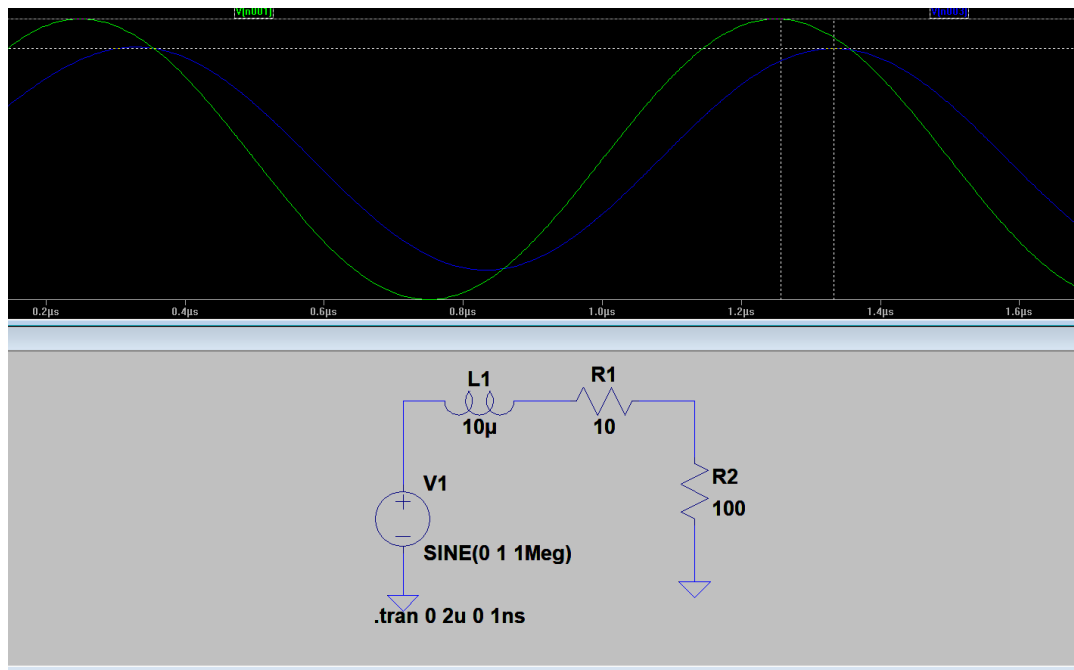
$$L = (R_1 - R_2) / \omega (\cot\phi_1 - \cot\phi_2)$$




(a1)

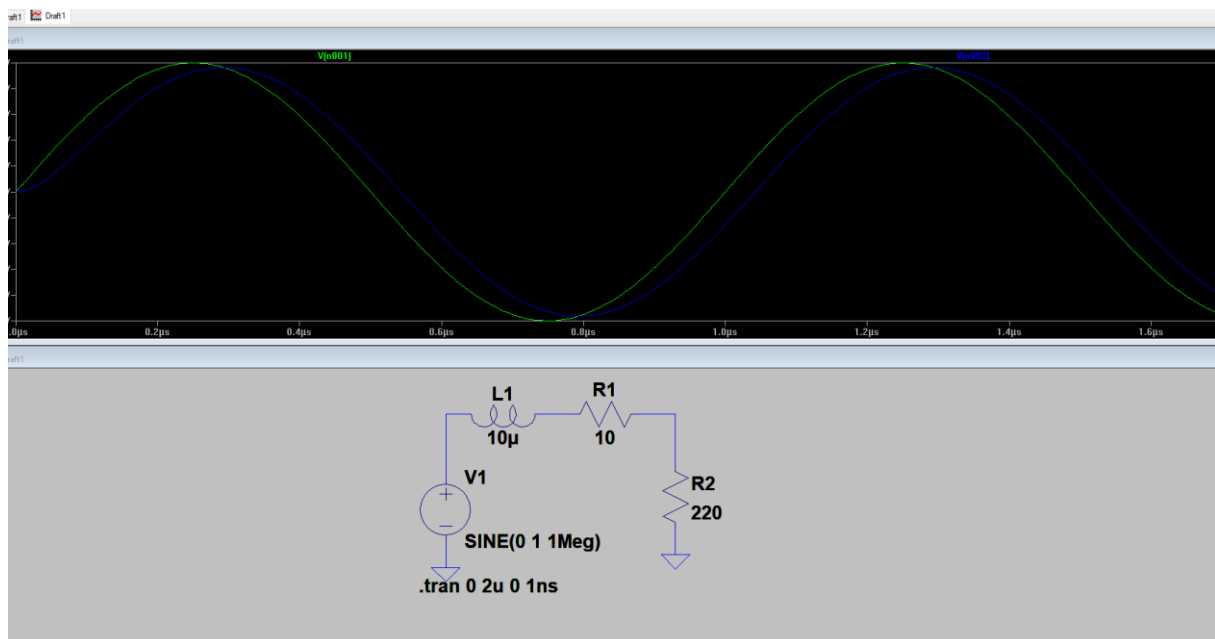First circuit which containing 100 ohm for R1 is in the figure a1. I have started my calculations from 1 MHz. And I have used 10 ohms for internal resistance of the inductor thinking it is a good approximation.



(a2)

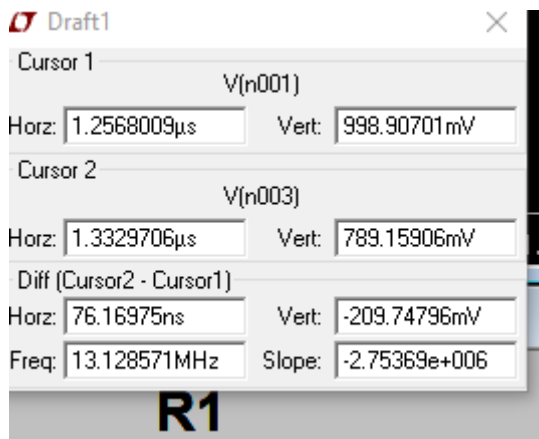In figure a2 the circuit two is shown which I have used 220 ohm for Rexternal.



(a3)

I have used cursors in LT spice to measure the time difference between two signals which I have later used the phase difference. Horizontal difference gave me the time difference between two circuits.

f	$\Delta t_1(\text{ns})$	$\Delta t_2(\text{ns})$	$\Delta \Theta_1$	$\Delta \Theta_2$	RI(ohm)	L(uh)
1	76.19	41.58	27.14	14.96	10.12	9.78
2	68.40	39.61	24.62	14.25	9.72	9.95
3	56.65	36.43	20.39	13.11	10.12	9.89
4	46.1	33.6	66.3	47.6	10.94	10.06

Qcalculated	Qexpected
6.06	6.28
12.64	12.35
18.41	18.84
23.1	25.13

My calculations showed me using phase difference to calculate quality factor is more reliable in lower frequency and as the frequency increases the error increases as well.

Java code I have written to make my calculations:

```
import java.util.Locale;
import java.util.Scanner;

public class Lab011
{
    public static void main(String args[])
    {
        Scanner scan = new Scanner(System.in).useLocale(Locale.US);

        double r1;

        double r2;

        double arl;

        double al;

        double f;

        double t1;

        double t2;

        System.out.print("R1: ");
        r1 = scan.nextDouble();
        System.out.println();

        System.out.print("R2: ");
        r2 = scan.nextDouble();
        System.out.println();

        System.out.print("AR1: ");
        arl = scan.nextDouble();
        System.out.println();

        System.out.print("AL: ");
        al = scan.nextDouble();
        System.out.println();

        System.out.print("t1: ");
        t1 = scan.nextDouble();
        System.out.println();

        System.out.print("t2: ");
        t2 = scan.nextDouble();
        System.out.println();

        System.out.print("F: ");
        f = scan.nextDouble();
```

```

System.out.println();

double dq1= -t1*360*0.001*f;

double dq2= -t2*360*0.001*f;

double q1= Math.toRadians(dq1);

double q2= Math.toRadians(dq2);

double L= -(r1-r2)/(6.28*((1/Math.tan(q1))-(1/Math.tan(q2))));

double r1=((Math.tan(q2))*r2-Math.tan(q1)*r1)/(Math.tan(q1)-Math.tan(q2));

double rerror = 100*(L-al)/(al);

double rerror = 100*(r1-ar1)/ar1;

double qexpected = (6.28*al)/ar1;

double qcalculated = (6.28*L)/r1;

System.out.println("L " + L);

System.out.println("RL " + r1);

System.out.println("rerror " + rerror);

System.out.println("qexpected " + qexpected);

System.out.println("qcalculated " + qcalculated);

}

```

## Second Method(Gain Ratio Method)

In this method the relation between  $R_{\text{external}}$  ,  $R_{\text{internal}}$  ,inductance and gain ratio is used to find quality factor.

$$(V_s/V_r)^2 = ((W L)^2 + (R_l + R_{\text{ext}})^2)/R_{\text{ext}}^2 = x$$

From this calculation I have calculated to x:  $x_1$  and  $x_2$  with two different external resistors.

$$R_l = ((r_1^2 * x_1) - ((R_l + r_1)^2 / (w^2)))$$

$$L = (x_1 * R_l^2 - (R_l + R_1)^2 / w^2)^{1/2}$$

I have used the same circuit I have used for method 1 so signals can be referred to  $a_1$  and  $a_2$  figures mentioned above.  $R_{\text{external}}$ s are also used as 100 and 220 same as the method 1.

f	Vs1	Vs0	Vs2	Vs02	RI	L	Q
1	999.2	767.3	998.5	930.1	10.4	12.5	7.1
2	999.7	602.5	999.2	842.3	10.3	10.1	12.2
3	999.8	455.1	999.6	740.6	10.2	9.9	18.2
4	999.7	360.8	999.8	650.2	10.5	9.9	23.6

## Java code I wrote for calculating method2

```
import java.util.Scanner;
import java.lang.Math;
import java.util.Locale;
public class Lab012
{
    public static void main(String args[])
    {
        Scanner scan = new Scanner(System.in).useLocale(Locale.US);

        // Input
        double r1;
        double r2;
        double arl;
        double al;
        double vs1;
        double v01;
        double vs2;
        double v02;
        double f;

        // Output
        double x1;
        double x2;
        double rL;
        double l;
        double rLError;
        double lError;
        double qExpec;
        double qCalculated;
        String selection = "";
        while(!selection.equals("e")){
            // Input
            System.out.print("R1: ");
            r1 = scan.nextDouble();
            System.out.println();
            System.out.print("R2: ");
            r2 = scan.nextDouble();
```

```

System.out.println();

System.out.print("AR1: ");
arl = scan.nextDouble();

System.out.println();

System.out.print("AL: ");
al = scan.nextDouble();

System.out.println();

System.out.print("VS1: ");
vs1 = scan.nextDouble();

System.out.println();

System.out.print("V01: ");
v01 = scan.nextDouble();

System.out.println();

System.out.print("VS2: ");
vs2 = scan.nextDouble();

System.out.println();

System.out.print("V02: ");
v02 = scan.nextDouble();

System.out.println();

System.out.print("F: ");
f = scan.nextDouble();

System.out.println();

// Output

x1 = Math.pow(vs1,2) / Math.pow(v01,2);
x2 = Math.pow(vs2,2) / Math.pow(v02,2);

rL = (Math.pow(r1,2)*(x1 - 1) - Math.pow(r2,2)*(x2 - 1))/(2*(r1 - r2));

l = Math.sqrt((Math.pow(r1,2)*x1-Math.pow(rL + r1,2))/Math.pow(2*Math.PI*f,2));

rLError = -((rL - arl)/arl)*100;

lError = ((l - al)/al)*100;

qExpec = (2*Math.PI*f*al)/arl;

qCalculated = (2*Math.PI*f*l)/rL;

// Print Output

System.out.println("-----");
System.out.println("-----");

System.out.println("X1: " + x1);
System.out.println("X2: " + x2);
System.out.println("RL: " + rL);
System.out.println("L: " + l);
System.out.println("RLError: " + rLError);

```

```

System.out.println("Lerror: " + lError);

System.out.println("Qexpec: " + qExpec);

System.out.println("Qcalculated: " + qCalculated);

System.out.println("-----");

System.out.println("-----");

// Exit, continue

System.out.println("for exit 'e', for continue 'c'");

selection = scan.next();

}

}

}

```

## Hardware Lab

### Toroidal Core

I have started the lab with Toroidal core because it was easier to find a fabricated inductor from the lab. After many tries I have made a toroidal inductor with the value of 4.35 uh and found a 10uh fabricated inductor from the lab.




b.1 my measurement of the toroidal inductor.

Toroid I have made. I have used core T-38 and 11 winding.


Below is given the measurement table for toroidal core method1



f	$\Delta t_1$	$\Delta t_2$	Rl	L	Q
1	76.3	27.5	3.95	5.0	7.6
2	56.3	16.7	4.2	5.4	15.9
3	40.7	11.2	4.0	5.2	24.4
4	32.5	8.3	4.4	5.0	28.5

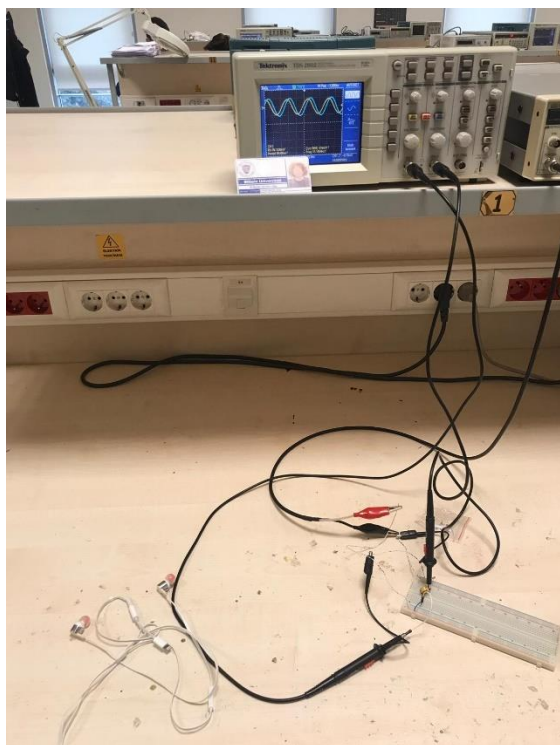


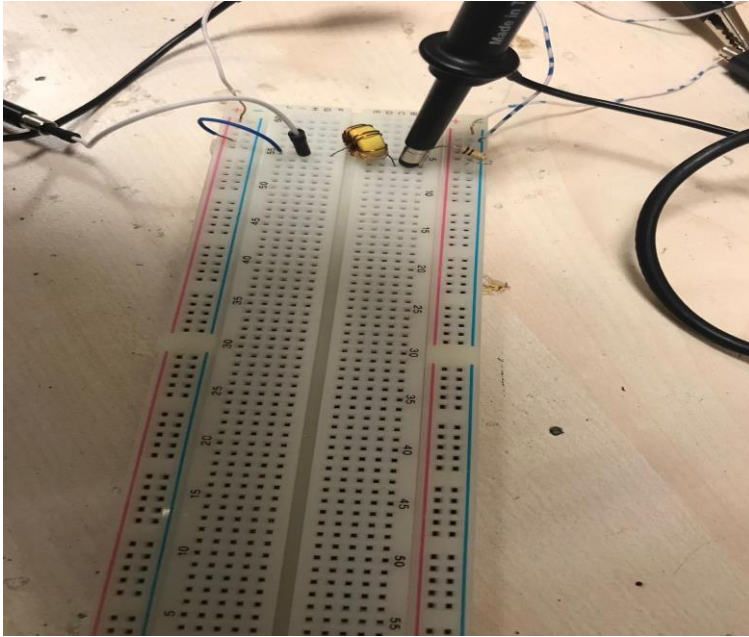b.2 experiment set up for toroidal inductor


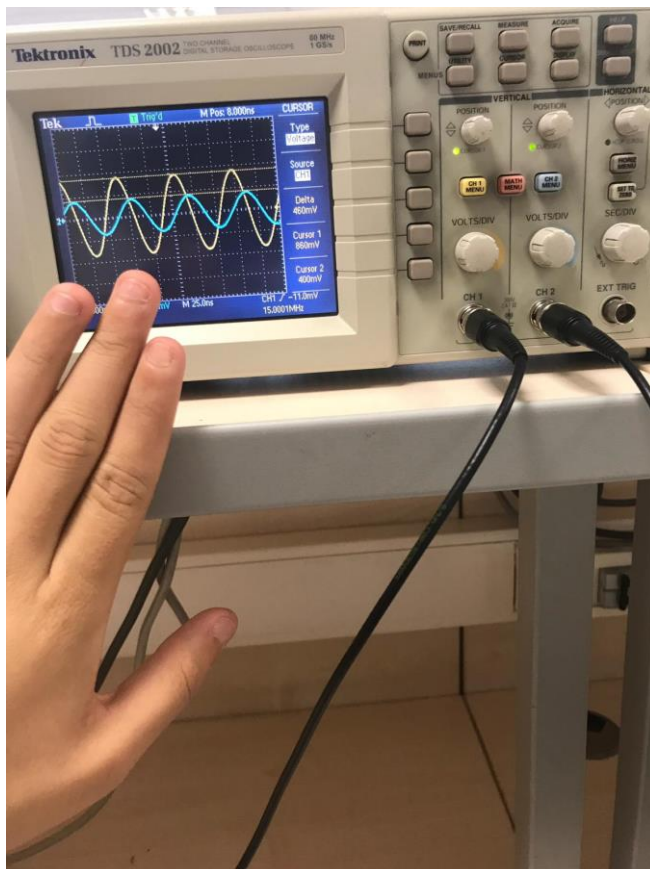
### b.3 circuit set up for toroidal inductor

Then I used gain ratio method for the same circuit this time using peak voltage values of the signals. I turned cursor to voltage mode and noted the peak voltages.



### b.4 Gain Ratio method oscilloscope result


f	Vs1	Vs0	Vs2	Vs02	Rl	L	Q
1	860,2	400,1	920,8	340,4	4.2	4.6	6.87
2	900,3	364,3	912,6	322.9	3,9	5,1	16.32
3	906.4	403.2	934.6	398.4	3.2	4.9	28.8
4	922.5	320.2	930.2	560.9	3.6	4.2	29.3

### **Fabricated Inductor Experiment**

After I was finished with the toroidal core experiment I used fabricated inductor with 10uH and it gave more reliable results compared to toroidal core inductor.

Below are given the measurements which had been taken for 10uh inductor and method 1 (phase difference) used to calculations.

f	$\Delta t_1$	$\Delta t_2$	Rl	L	Q
1	96.2	50.1	2.1	10.9	32.5
2	75.3	48.4	2.6	11.4	55.6
3	61.1	43.7	1.8	11.3	118.27
4	48.3	37.1	2.1	11.6	138.7

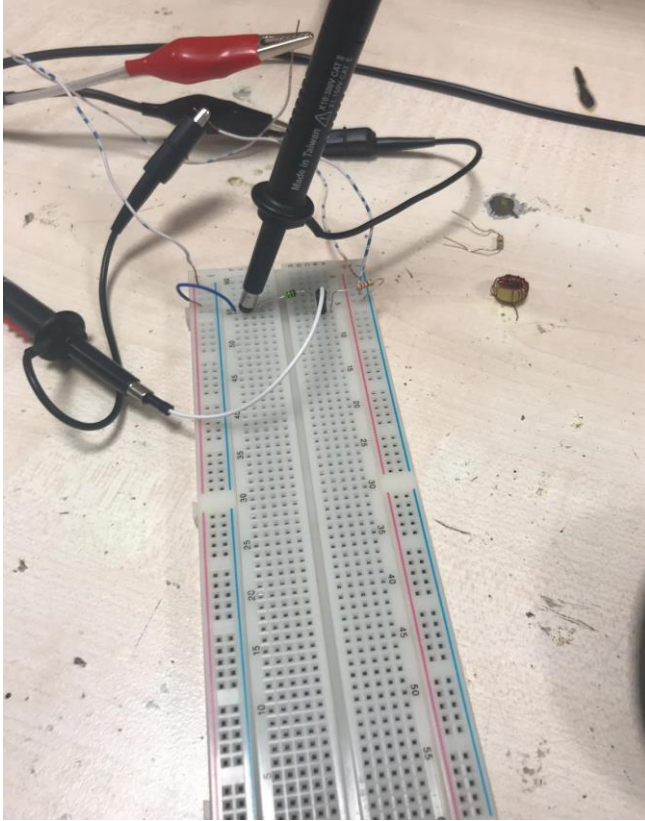

#### b.4 circuit setup for fabricated inductor

I used the same circuit for method2( Gain ratio method). Below are my result table for fabricated inductor circuit and gain ratio method.

f	Vs1	Vs0	Vs2	Vs02	Rl	L	Q
1	716	538	1550	1480	2.4	11.3	29.5
2	840	460	870	726	2.9	11.5	49.4
3	910	380	920	654	2.5	9.4	70.8
4	930	300	910	550	1.6	10.6	166.4

#### Conclusion

In this lab two methods was needed to calculate quality factor (Q) thus inductance and internal resistance needed to be find in order to calculate Q because of the  $Q = \omega * L / R_l$ . Gain ratio method used voltage relationship between input and output signals of the inductor. Phase

difference method used time difference between the input and output signals of the inductor. Because of the variable insufficiency two resistors are used to create two equations and solve it for two unknowns. In software lab I used Ltspice and java. Ltspice is used for simulating the circuit which I have designed then java is used to make the calculations easier for both methods. In hardware lab I used breadboard , fabricated inductor with 10uh and toroidal core inductor with 4.5uh. I have used the methods with on my circuit and it was successful. Toroidal core error rate was higher I think it was because of the hand winding is not reliable compared to fabricated inductor. Lab goals which was assigned was completed.